



ECSE 325

LAB 5 REPORT

Martin Kruchinski Almeida
(260915767)
Menad Kessaci
(260807381)

Group 35



G35_timestamper System:

Introduction – Description of the circuit:

In this lab, we worked on the creation of a circuit that acts as a time-stamper. The circuit takes a message from a source, generates a time-stamp for it, and affixes a digital signature to the message. Then, the circuit outputs a digital signature.

Formally speaking, the time-stamper circuit has 4 inputs: a clock signal, a reset signal, an enable signal, a message, and a timestamp. The clock, the reset and the enable signals are all 1-bit signals. The message is a 32-bit vector while the timestamp is a 22-bit vector representing the number of hours since year 2000. The circuit has 1 output: a signature that is 16-bits wide.

It is worth noting that the timestamp used as an input for the time-stamper is generated by another circuit: g35_Hash10. In summary, the latter takes a message and produces a hash for the input message.

VHDL Testbench code:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
use ieee.numeric_std.all; -- needed if you are using unsigned numbers
ENTITY g35_timestamper_vhd_tst IS
END g35_timestamper_vhd_tst;
ARCHITECTURE g35_timestamper_arch OF g35_timestamper_vhd_tst IS
-- constants
-- signals
SIGNAL clk : STD_LOGIC;
SIGNAL enable : STD_LOGIC;
SIGNAL message : STD_LOGIC_VECTOR(31 DOWNTO 0);
SIGNAL rst : STD_LOGIC;
SIGNAL signature : STD_LOGIC_VECTOR(15 DOWNTO 0);
SIGNAL timestamp : STD_LOGIC_VECTOR(21 DOWNTO 0);
COMPONENT g35_timestamper
PORT (
    clk : IN STD_LOGIC;
    enable : IN STD_LOGIC;
    message : IN STD_LOGIC_VECTOR(31 DOWNTO 0);
    rst : IN STD_LOGIC;
    signature : OUT STD_LOGIC_VECTOR(15 DOWNTO 0);
    timestamp : IN STD_LOGIC_VECTOR(21 DOWNTO 0)
);
END COMPONENT;
BEGIN

init : PROCESS
begin
    clk <= '0';
    wait for 5 ns;
    clk <= '1';
    wait for 5 ns;
end process;

i1 : g35_timestamper
PORT MAP (
-- list connections between master ports and signals
    clk => clk,
    enable => enable,
    message => message,
    rst => rst,
    signature => signature,
    timestamp => timestamp
);

always : PROCESS
BEGIN
    enable <= '0';
    message <= "0000000000000000000000000000000000000000000000000000000000000000";
    timestamp <= std_logic_vector(to_unsigned(19794,22));
    rst <= '1';
    wait for 10 ns;
    rst <= '0';
    enable <= '1';
    wait for 30 ns;
    message <= "0000000000001110000000000000000000000000000000000000000000000000";
WAIT;
END PROCESS always;
END g35_timestamper_arch;
```

Simulation results (all the results are unsigned decimals):

